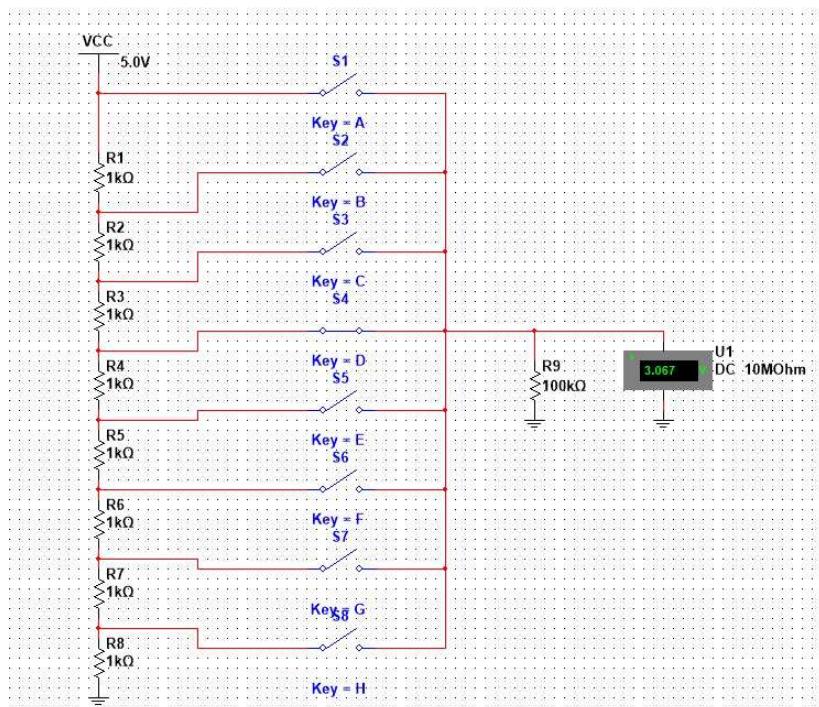




University of British Columbia  
Electrical and Computer Engineering  
Electrical and Biomedical Engineering Design Studio  
ELEC291/ELEC292

# Adding ADC Push Buttons to the N76E003 + LCD

Copyright © 2006-2024, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.



<b>Button</b>	<b>Voltage</b>	<b>ADC</b>	<b>Hex</b>	<b>Compare</b>
0	0.625	31	1F	10
1	1.250	63	3F	30
2	1.875	95	5F	50
3	2.500	127	7F	70
4	3.125	159	9F	90
5	3.750	191	BF	B0
6	4.375	223	DF	D0
7	5.000	255	FF	F0

